

CHALLENGER IP VIDEO DISPLAY MODIFICATIONS

Copyright C. 1979 by Steven Chalfin
905 Clinton Street
Phila., PA 19107

All Rights Reserved



INTRODUCTION:

The CHALLENGER IP (SUPERBOARD II) computer system is one of the best values in hobby computers today. Its many outstanding features are well known. However, its low price has necessitated several design compromises. One of these compromises involves the video display circuitry. The advertised 32x32 format is actually only 24x24 or at best 26x26 on a standard television. Even if a high quality monitor is used and the display size can be increased, the BASIC in ROM will still limit the line length to 24 characters.

Adding guard band circuitry would give a true 32x32 display on a standard television, but would be both expensive and technically difficult to implement. The most cost-effective solution this author has found, and the one which is described in this manual, is outlined below:

- 1) Double the dot clock frequency. This has the effect of putting out twice as many dots per scan line (twice as many characters per line).
- 2) Since there will be twice as many characters per line but the same number of lines on the screen, an additional 1K of video memory must be added.
- 3) Associated circuit changes for memory decoding, sync pulses, etc.
- 4) A software patch so that BASIC will use the entire screen to display.

These modifications yield a 32 line x 64 character display. Since this circuitry still lacks guard band capability, some characters are lost off the screen due to overscan. However, the resultant 30 line x 50 character display is a vast improvement.

It is assumed that the person undertaking this conversion is familiar with such basic electronic construction techniques as soldering and reading schematics. Components required for this conversion are:

| QUAN | DESCRIPTION |
|------|--|
| 4 | 2114 or 2114L 450nS or faster RAM* |
| 1 | 8.0 MHz crystal |
| 1 | 74LS163 or 74LS161 4 bit binary counter+ |
| 1 | 74LS139 2 to 4 decoder (dual)+ |
| 2 | 16 pin DIP sockets |

*This is critical! Don't buy slower (cheaper) RAMs as they will not work.

+Be sure to use the 74LS series, not the 74 series as these are slower and may not work.

Also required: Model 600 schematic, solder, #30 AWG wire wrap wire, soldering iron, wire stripper, razor blade or X-acto knife.

These parts may be had for \$40 or less, depending on how well stocked your junk box is.

STARTING ON THE RIGHT FOOT:

Unless you have absolute confidence in the quality control procedures of IC manufacturers you should test the parts which will be used in this conversion. The easiest way to do this is simply to substitute them for equivalent parts on the 600 board.

First, remove the six screws securing the bottom of the case. Then remove the six screws securing the 600 board to the top of the case. Carefully unplug the power and interface connectors and place the board on a clean work surface, component side up. Carefully remove U57 and replace it with your new 74LS163. Carefully remove U17 and replace it with your new 74LS139.

Carefully remove the video RAMs (U39, U40), which will not be used in the new circuitry, and replace with 2 of the new 2114's. Recheck the orientation of the new chips. Reconnect the 600 board. Turn on the power. Try reading programs by cassette, printing on the screen, etc. to make sure everything is working. Run a memory test program on the video RAM space 53248-54272 decimal or D000 to D3FF hex. A short, but slow program is shown below:

```
10 FOR I=53248 TO 54272:FOR J=0 TO 255  
20 POKE I,J:IF PEEK(I)<>J THEN STOP  
30 NEXT:NEXT I  
40 ?"OK"
```

BREAK IN 20 indicates a memory read or write error. If everything looks good remove the board again and replace the two new video RAMs with the two remaining new 2114's. Reinstall the board and rerun the memory test program. If everything checks out remove the board once again.

SPEEDING UP THE CLOCK:

Unsolder the crystal, X1. Install in its place the new 8.0 MHz crystal. Be sure to bend the leads so that the crystal is flat against the board.

This doubles the frequency of all clock lines on the board: CLK, C0-C15, ϕ_0 in, VS, HS, TxCLK. Since the microprocessor used in the CIP is a 6502A, which is rated to run at 2.0 MHz, this modification will also double the speed of your computer. The author has some reservations about running the CIP at 2 MHz, as this speed may be pushing the system RAMs (550nS) at their limit. The author's system has been running at this speed for over 150 hours with no apparent read or write errors, but in anticipation of individual variations in different CIP's a modification to return the speed to 1 MHz will be given.

MEMORY, SYNC, ETC.

The CIP uses multiplexer circuitry so that the video address lines may be connected either to the video circuitry or the system address buss. Normally, the video display memory is connected to the video circuitry. However, when the system address buss specifies an address between D000 and D3FF (hex), the multiplexer switches connection of the video address lines (VA0 - VA9) to the address buss.

Control of the video RAM is directed by lines: \overline{WVE} , \overline{RVE} , \overline{MCS} , \overline{VA} . Since the video RAM will be expanded to occupy addresses D000 - D7FF (hex) the address decoding for the above mentioned signals must be altered accordingly.

Refer to FIG 1:

- 1) Cut the ($\overline{A10}$) trace to U20 pin 1.
- 2) Connect U20 pin 1 to the adjacent Vcc buss.
- 3) Cut the (\overline{WKB}) trace to U20 pin 11.
- 4) Connect the previously cut (\overline{WKB}) trace to U20 pin 10.
- 5) Cut the (\overline{RKB}) trace at the point shown, where it runs next to the GND buss.
- 6) Connect the previously cut (\overline{RKB}) trace to U20 pin 14.

Be sure that all cut traces are cut all the way through. An easy way to do this is to make two parallel cuts across the trace approximately 1/16th of an inch apart. Then, with the point of your blade, scrape off the small piece between the cuts.

Also, try to keep your wires as short and direct as possible.

Refer to FIG 2:

- 7) Cut the ($\overline{A10}$) trace on the component side of the board at the plated through hole, where it emerges just under the rightmost prototyping area (U26).

Not shown:

- 3) Connect U56 pin 1 and U56 pin 2 together on the foil side of the board.

Refer to FIG 3:

- 9) Cut the (C7) trace from U59 pin 11 at the plated through hole on the component side of the board as shown just above and to the left of U59.

- 10) Cut the (C11) trace from U54 pin 6 at the plated through hole just above U54, as shown.

Refer to FIG 4:

- 11) Cut the (GND) trace to U55 pin 10 on the foil side of the board.
- 12) Cut the (~~C2~~) trace where it runs next to the GND buss just above U41, the character generator ROM.
- 13) Solder two 16 pin DIP sockets in the two rightmost prototyping areas (U26, U27).
- 14) Connect U26 pin 8 to the GND buss. Connect U26 pin 16 to the Vcc buss.
- 15) Connect U27 pin 8 to the GND buss. Connect U27 pin 1 to the Vcc buss.
- 16) Using short pieces of wire, connect U26 pins 3, 8, 14, and 15 together.
- 17) Using short pieces of wire, connect U27 pins 3, 4, 5, 6, and 8 together.
- 18) Connect the previously cut (~~C2~~) trace to U26 pin 1, as shown.
- 19) Connect U55 pin 10 to U26 pin 12.
- 20) Connect U55 pin 11 to U26 pin 5.
- 21) Connect U55 pin 13 to U26 pin 10.
- 22) Connect U55 pin 14 to U26 pin 4.
- 23) Connect U26 pin 2 to the (~~A10~~) trace which runs directly below the Vcc buss under U26, as shown.
- 24) Connect U26 pin 13 to U27 pin 14.
- 25) Connect U27 pins 9 and 16 together and to the Vcc buss directly under U27.
- 26) Connect U27 pin 10 to U61 pin 15.
- 27) Connect U27 pin 2 to U30 pin 2.
- 28) Connect U27 pin 14 to U65 pin 1.
- 29) Connect U27 pin 7 to U30 pin 15.
- 30) Connect U60 pin 14 to U54 pin 6.
- 31) Connect U60 pin 14 to the trace which runs directly below the topmost Vcc buss on the board, as shown.
- 32) Connect U41 pin 6 to the (C11) trace which runs between the two plated through holes above U54, as shown.
- 33) Cut the (C4) trace which runs just above the GND buss over U54, as shown.
- 34) Connect the previously cut (C4) trace to U59 pin 13.
- 34a) Cut the (C15) trace to U65 pin 1 at that pin

Refer to FIG 5:

- 35) Cut the three (C10), (C9), (C8) traces to U41 pins 6, 7, and 8.
- 36) Connect the middle (C9) trace to U41 pin 8.
- 37) Connect the right (C10) trace to U41 pin 7. Leave the left (C8) trace unconnected.

Refer to FIG 6:

- 38) Making very sure to correctly orient them in the same direction, piggyback two of the new 2114L memory chips as shown. Be absolutely certain that all pins of the top chip are in contact with the corresponding pins on the lower chip, except pin 8. Bend pin 8 of the upper chip away from pin 8 of the lower chip.

Carefully, using a low wattage iron, solder all corresponding pins of the upper & lower chips together (except, as noted above, pins 8).

Solder a 6" length of ww wire to pin 8 of the upper chip as shown.

- 39) Repeat step (38) for the remaining two new 2114L's.
- 40) Making sure they are oriented correctly, insert the two piggy-backed 2114L assemblies into sockets U39 and U40.
- 41) Route the two wires from pin 8 through the nearest plated through holes to the foil side of the board and connect them to U55 pin 12.
- 42) Insert the 74LS139 into socket U26. Be sure orientation is correct.
- 43) Insert the 74LS163 into socket U27. Be sure orientation is correct.

This completes the hardware modifications to your CIP. Recheck all connections to insure they are correct. Make especially sure that pin 8 of the upper and lower 2114L's do not touch.

Reinstall the circuitboard and reconnect the power and interface connectors. Turn on the television and then the CIP. The screen should fill with random characters. Some adjustment of Horiz, Vert, Bright, and Cont may be necessary to obtain the best picture.

If the screen remains dark or if standard characters are not seen, remove power immediately and recheck all wiring.

Best picture quality and the most characters per line are obtained by direct connection of the CIP video signal to your television's video amplifier stage. This bypasses the sound trap and some of the lower bandwidth sections of the television. This modification is described in many computer magazines and will not be covered here. Also, try decreasing the low voltage control of your set as this may allow you to fit more characters per line.

Software:

The subroutine which runs the video display on the C1P is located in BASIC ROM 4, at address BF2D (hex). Since OSI uses this ROM in several of their computers, the subroutine relies on parameters located in the monitor PROM to determine the number of characters per line. These are as follows:

| <u>LOCATION</u> | <u>VALUE</u> | <u>FUNCTION</u> |
|-----------------|--------------|--|
| FFE0 | 65 | Position of cursor after CR, LF. |
| FFE1 | 17 | Characters per line - 1. |
| FFE2 | 00 | Video memory size. (00 = 1K, any other number = 2K). |

If one has the capability to program PROMs, the most elegant way to reset the display parameters is to simply program a duplicate monitor ROM, changing as necessary the above three addresses. Most of us, however, lack this capability and must resort to a software patch. The patch given below is essentially the same as the BASIC subroutine, but since it is in RAM, the line length, cursor position etc. may be user specified. In addition, it contains a machine language screen clear function so that a ?CHR\$(1) will give a fast screen clear.

This is a fairly long patch, and storing it in RAM via the monitor is prohibitively time consuming. I would therefore recommend that you save it on tape in monitor loadable format the first time you load it and are sure all is well. A good program for saving machine code programs on tape may be found in the April, 1979 issue of MICRO magazine. When placed on tape in this format, the patch takes only 19 seconds to load.

In order for this patch to work the output vector, located at 021A and 021B (hex) must be changed from FF69 to 0222, the start address of the patch. It should be noted that this vector is reset to FF69 every time the reset key is pressed, so a reset will necessitate reloading it with 0222. A nice feature to minimize the amount of keyboard entry is to modify the aforementioned machine language save program to output .BDLLG after the patch. This will obviate the need to reset and reload the patch start address into the output vector and will automatically cold start BASIC.

This patch is relocatable, although it will require some changes. I recommend leaving it at 0222 as this area in RAM is not used by BASIC.

With this patch in operation, the video display will consist of 30 lines (2 are lost off the top edge of the screen) by 50 to 52 characters (12 to 14 are lost in overscan).

PATCH:

| | | | | | |
|------|----|----|----|-----------|---------------|
| Ø222 | 8D | Ø2 | Ø2 | STA Ø2Ø2 | |
| Ø225 | 48 | | | PHA | |
| Ø226 | 8A | | | TXA | |
| Ø227 | 48 | | | PHA | |
| Ø228 | 98 | | | TYA | |
| Ø229 | 48 | | | PHA | |
| Ø22A | AD | Ø2 | Ø2 | LDA Ø2Ø2 | |
| Ø22D | FØ | 4C | | BEQ 4C | |
| Ø22F | AC | Ø6 | Ø2 | LDY Ø2Ø6 | |
| Ø232 | FØ | Ø8 | | BEQ Ø8 | |
| Ø234 | A2 | 4Ø | | LDX 4Ø | |
| Ø236 | CA | | | DEX | |
| Ø237 | DØ | FD | | BNE FD | |
| Ø239 | 88 | | | DEY | |
| Ø23A | DØ | F8 | | BNE F8 | |
| Ø23C | C9 | ØA | | CMP ØA | Linefeed? |
| Ø23E | FØ | 46 | | BEQ 46 | |
| Ø24Ø | C9 | Ø1 | | CMP Ø1 | Screen clear? |
| Ø242 | DØ | 1A | | BNE 1A | |
| Ø244 | A9 | 2Ø | | LDA 2Ø | |
| Ø246 | AØ | Ø8 | | LDY Ø8 | |
| Ø248 | A2 | ØØ | | LDX ØØ | |
| Ø24A | 9D | ØØ | DØ | STAX DØØØ | |
| Ø24D | E8 | | | INX | |
| Ø24E | DØ | FA | | BNE FA | |
| Ø25Ø | EE | 4C | Ø2 | INC Ø24C | |
| Ø253 | 88 | | | DEY | |
| Ø254 | DØ | F4 | | BNE F4 | |
| Ø256 | A9 | DØ | | LDA DØ | |
| Ø258 | 8D | 4C | Ø2 | STA Ø24C | |
| Ø25B | 4C | 7B | Ø2 | JMP Ø27B | |
| Ø25E | C9 | ØD | | CMP ØD | |
| Ø26Ø | DØ | Ø6 | | BNE Ø6 | |
| Ø262 | 2Ø | D2 | Ø2 | JSR Ø2D2 | |
| Ø265 | 4C | 7B | Ø2 | JMP Ø27B | |
| Ø268 | 8D | Ø1 | Ø2 | STA Ø2Ø1 | |
| Ø26B | 2Ø | C8 | Ø2 | JSR Ø2C8 | |
| Ø26E | EE | ØØ | Ø2 | INC Ø2ØØ | |
| Ø271 | A9 | F9 | | LDA F9* | |
| Ø273 | CD | ØØ | Ø2 | CMP Ø2ØØ | |
| Ø276 | 3Ø | ØB | | BMI ØB | |
| Ø278 | 2Ø | DA | Ø2 | JSR Ø2DA | |
| Ø27B | 68 | | | PLA | |
| Ø27C | A8 | | | TAY | |
| Ø27D | 68 | | | PLA | |
| Ø27E | AA | | | TAX | |
| Ø27F | 68 | | | PLA | |
| Ø28Ø | 4C | 6C | FF | JMP FF6C | |

Linefeed?

Screen clear?

Screen clear subroutine.

Carriage Return?

| | | | | | |
|------|----|----|----|------|------|
| Ø283 | 2Ø | D5 | Ø2 | JSR | Ø2D5 |
| Ø286 | 2Ø | C8 | Ø2 | JSR | Ø2C8 |
| Ø289 | A9 | BF | | LDA | BF+ |
| Ø28B | EA | | | NOP | |
| Ø28C | EA | | | NOP | |
| Ø28D | 8D | Ø2 | Ø2 | STA | Ø2Ø2 |
| Ø29Ø | A2 | Ø7 | | LDX | Ø7 |
| Ø292 | BD | F3 | BF | LDAX | BFF3 |
| Ø295 | 9D | Ø7 | Ø2 | STAX | Ø2Ø7 |
| Ø298 | CA | | | DEX | |
| Ø299 | 1Ø | F7 | | BPL | F7 |
| Ø29B | A2 | D7 | | LDX | D7 |
| Ø29D | A9 | 4Ø | | LDA | 4Ø |
| Ø29F | 8D | Ø8 | Ø2 | STA | Ø2Ø8 |
| Ø2A2 | AØ | ØØ | | LDY | ØØ |
| Ø2A4 | 2Ø | Ø7 | Ø2 | JSR | Ø2Ø7 |
| Ø2A7 | DØ | FB | | BNE | FB |
| Ø2A9 | EE | Ø9 | Ø2 | INC | Ø2Ø9 |
| Ø2AC | EE | ØC | Ø2 | INC | Ø2ØC |
| Ø2AF | EC | Ø9 | Ø2 | CPX | Ø2Ø9 |
| Ø2B2 | DØ | FØ | | BNE | FØ |
| Ø2B4 | 2Ø | Ø7 | Ø2 | JSR | Ø2Ø7 |
| Ø2B7 | CC | Ø2 | Ø2 | CPY | Ø2Ø2 |
| Ø2BA | DØ | F8 | | BNE | F8 |
| Ø2BC | A9 | 2Ø | | LDA | 2Ø |
| Ø2BE | 2Ø | ØA | Ø2 | JSR | Ø2ØA |
| Ø2C1 | CE | Ø8 | Ø2 | DEC | Ø2Ø8 |
| Ø2C4 | DØ | F8 | | BNE | F8 |
| Ø2C6 | FØ | AE | | BEQ | AE |
| Ø2C8 | AE | ØØ | Ø2 | LDX | Ø2ØØ |
| Ø2CB | AD | Ø1 | Ø2 | LDA | Ø2Ø1 |
| Ø2CE | 9D | ØØ | D7 | STAX | D7ØØ |
| Ø2D1 | 6Ø | | | RTS | |
| Ø2D2 | 2Ø | C8 | Ø2 | JSR | Ø2C8 |
| Ø2D5 | A9 | C8 | | LDA | C8# |
| Ø2D7 | 8D | ØØ | Ø2 | STA | Ø2ØØ |
| Ø2DA | AE | ØØ | Ø2 | LDX | Ø2ØØ |
| Ø2DD | BD | ØØ | D7 | LDAX | D7ØØ |
| Ø2EØ | 8D | Ø1 | Ø2 | STA | Ø2Ø1 |
| Ø2E3 | A9 | 5F | | LDA | 5F |
| Ø2E5 | DØ | E7 | | BNE | E7 |

Output Vector: Ø21A 22 Ø2

Cold Start: .BD11 G

Warm Start: .A274 G

* Cursor starting position + no of characters per line - 1.




+ Cursor starting position - no of characters lost in left overscan.

Cursor starting position.

BACK TO 1MHz:

Should you find that the system RAM is not performing adequately at 2MHz, you can return the processor clock to 1 MHz by:

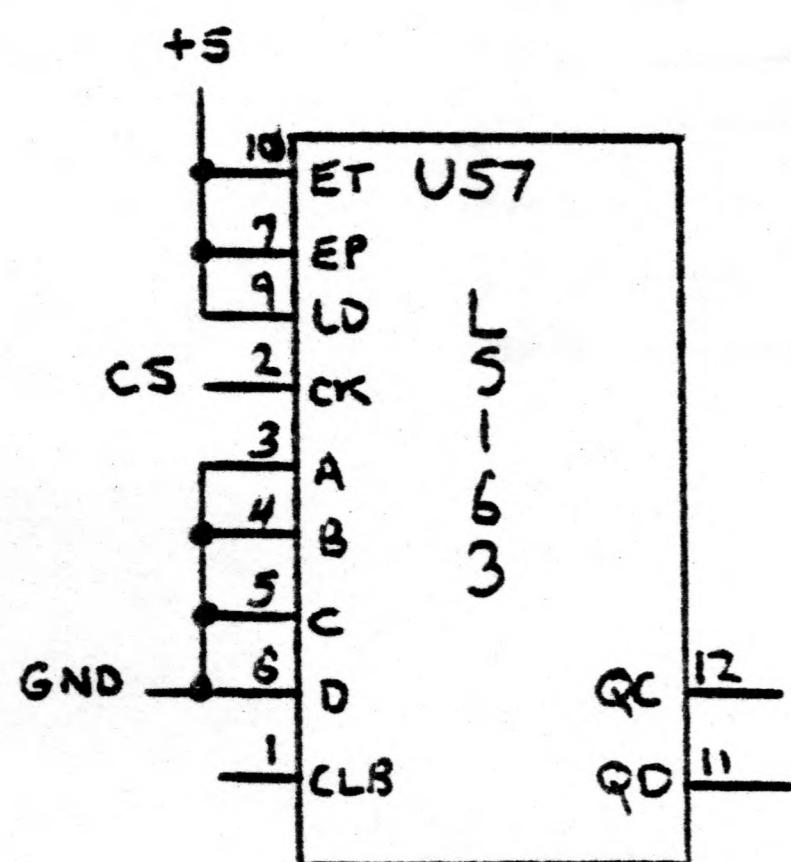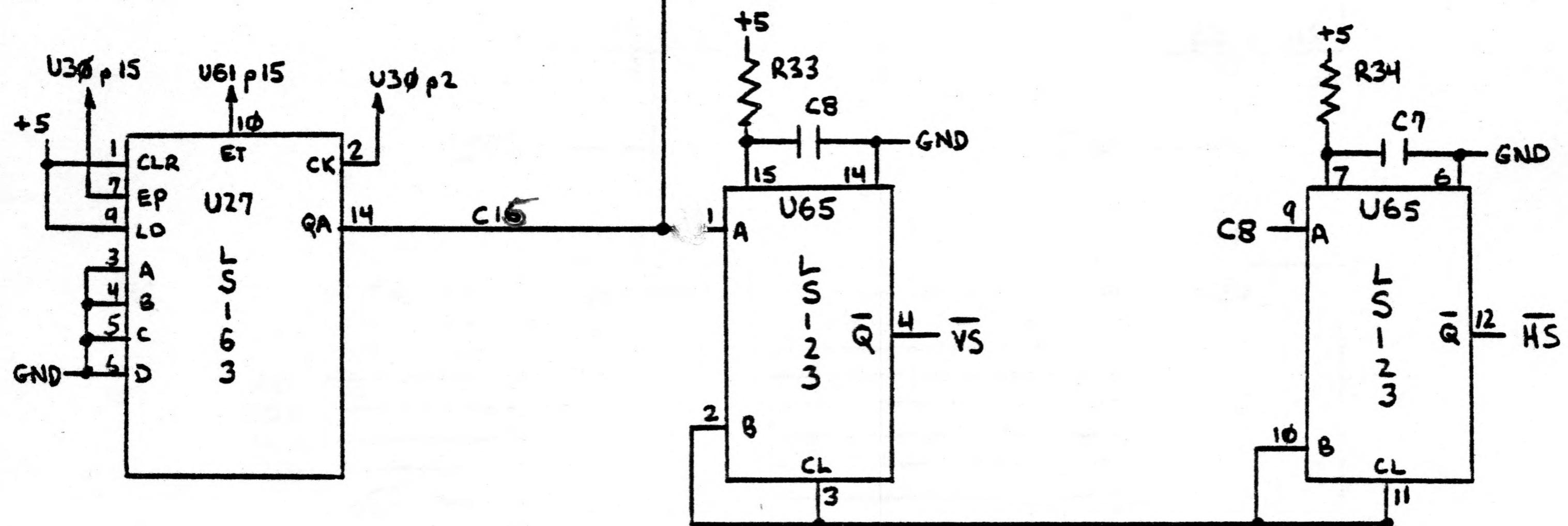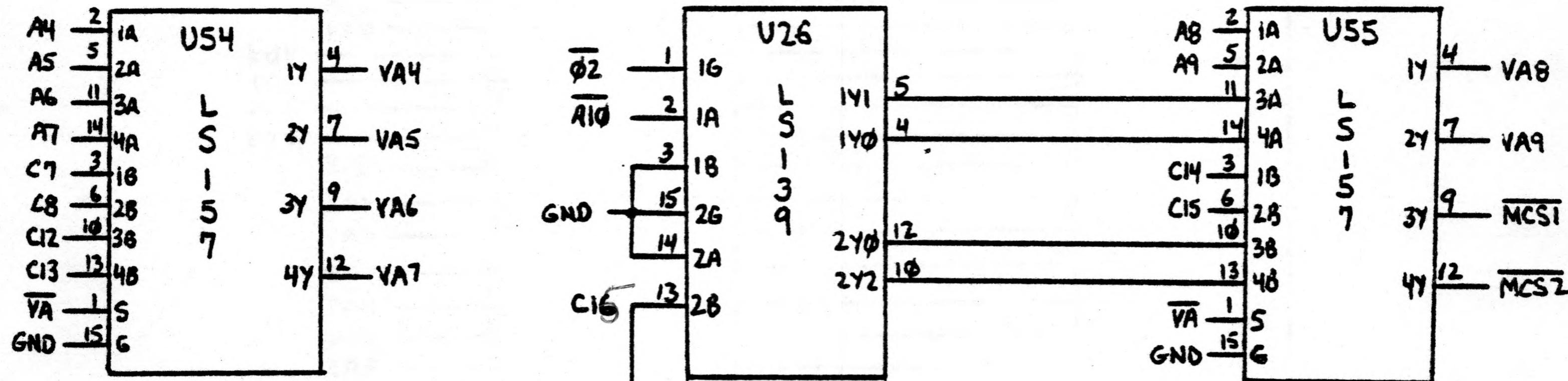- 1) On the component side of the board, cut the (ϕ 0in) trace to U8 pin 37.
- 2) Connect U8 pin 37 to U30 pin 12.



| | 18 | 20 | 21 | |
|-----|----|-----|------|-----|
| VD0 | 5 | A3 | S1 | D0 |
| VD1 | 4 | A4 | S2 | D1 |
| VD2 | 3 | A5 | S3 | D2 |
| VD3 | 2 | A6 | CHAR | D3 |
| VD4 | 1 | A7 | GEN | D4 |
| VD5 | 23 | A8 | | D5 |
| VD6 | 22 | A9 | | D6 |
| VD7 | 19 | A10 | | D7 |
| C9 | 8 | A0 | | A1 |
| | | | | A2 |
| | | | | C11 |
| | | | 7 | |
| | | | C10 | |

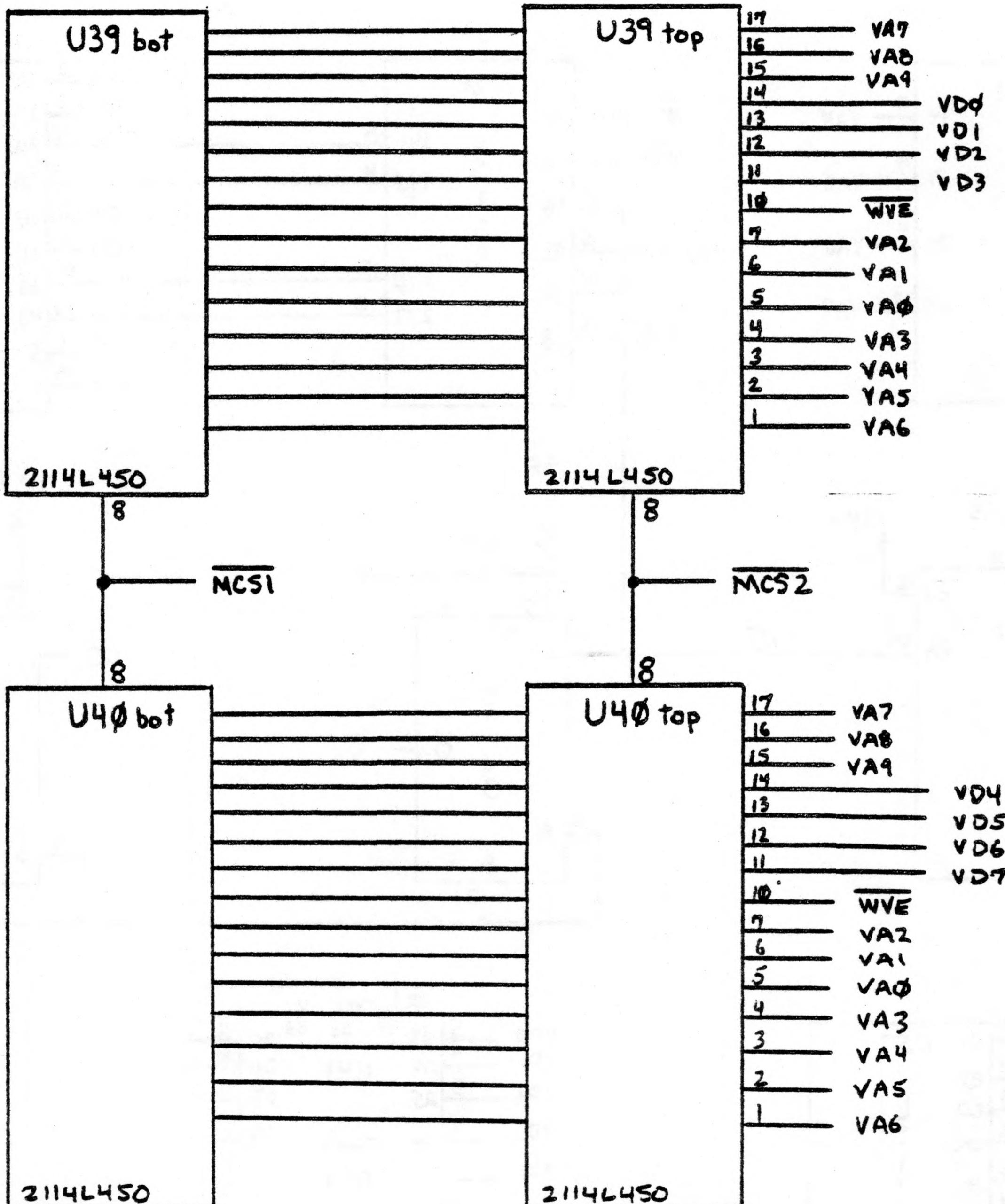
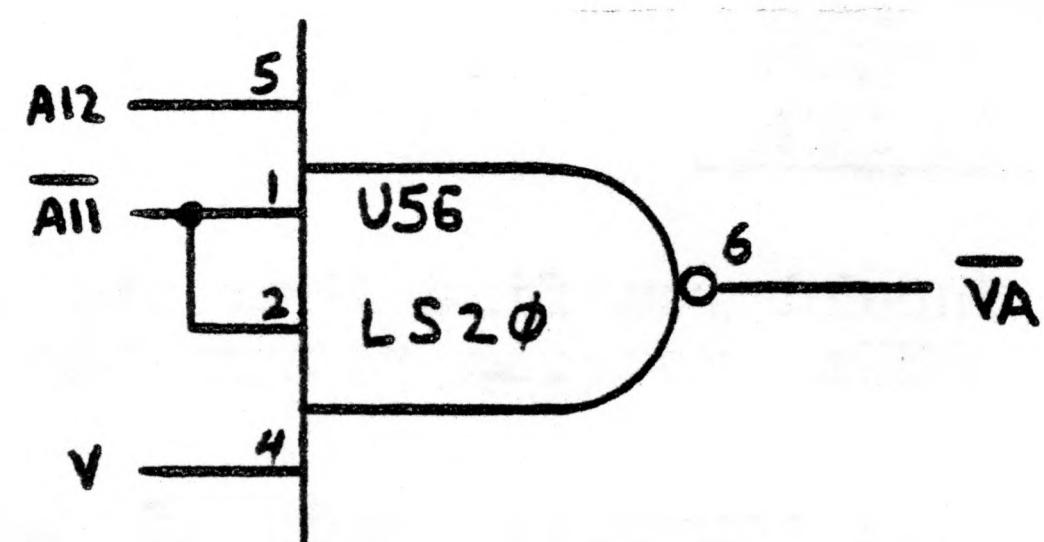
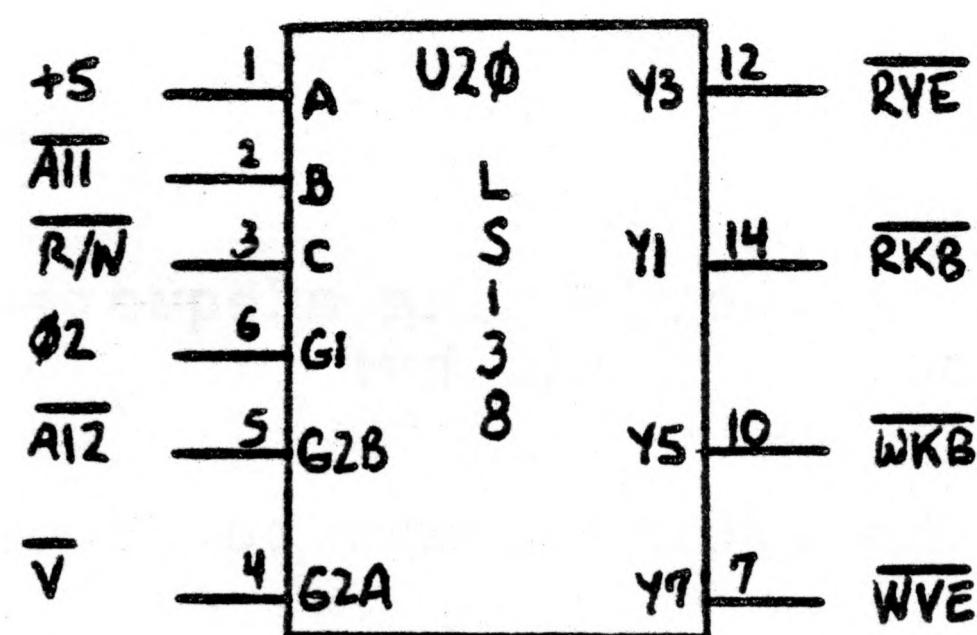


FIG 1
FOIL SIDE

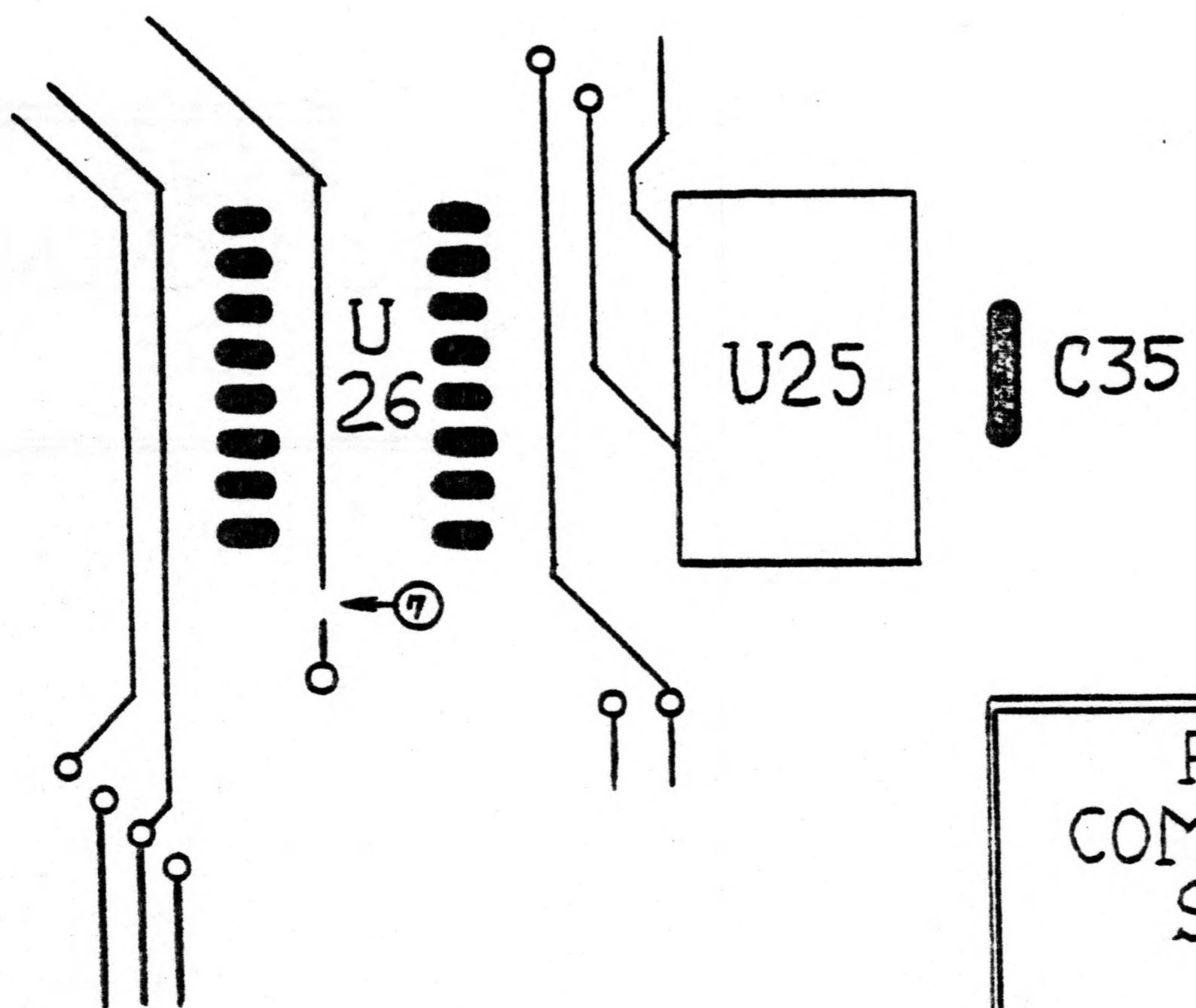
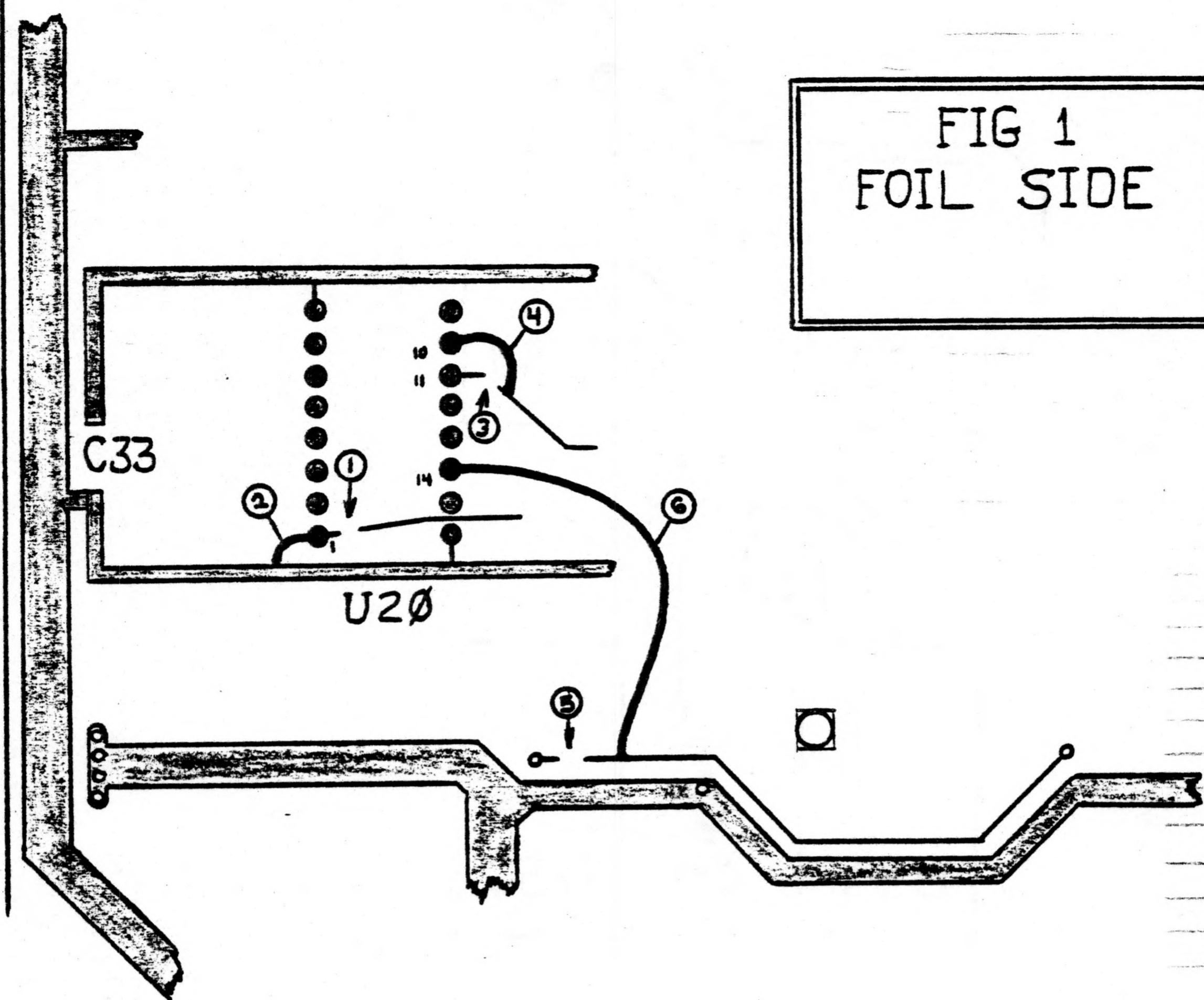


FIG 2
COMPONENT
SIDE


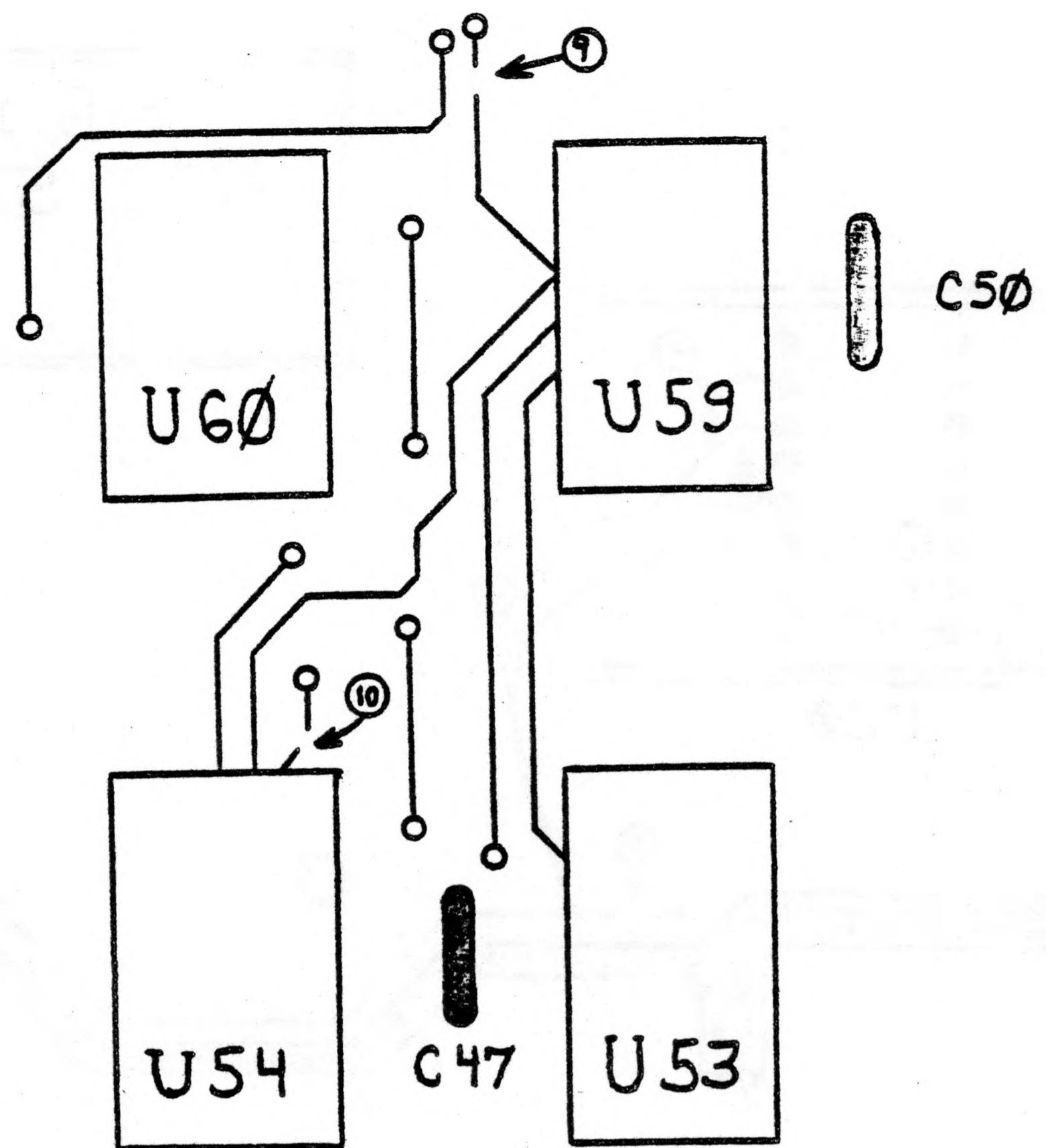


FIG 3
COMPONENT
SIDE

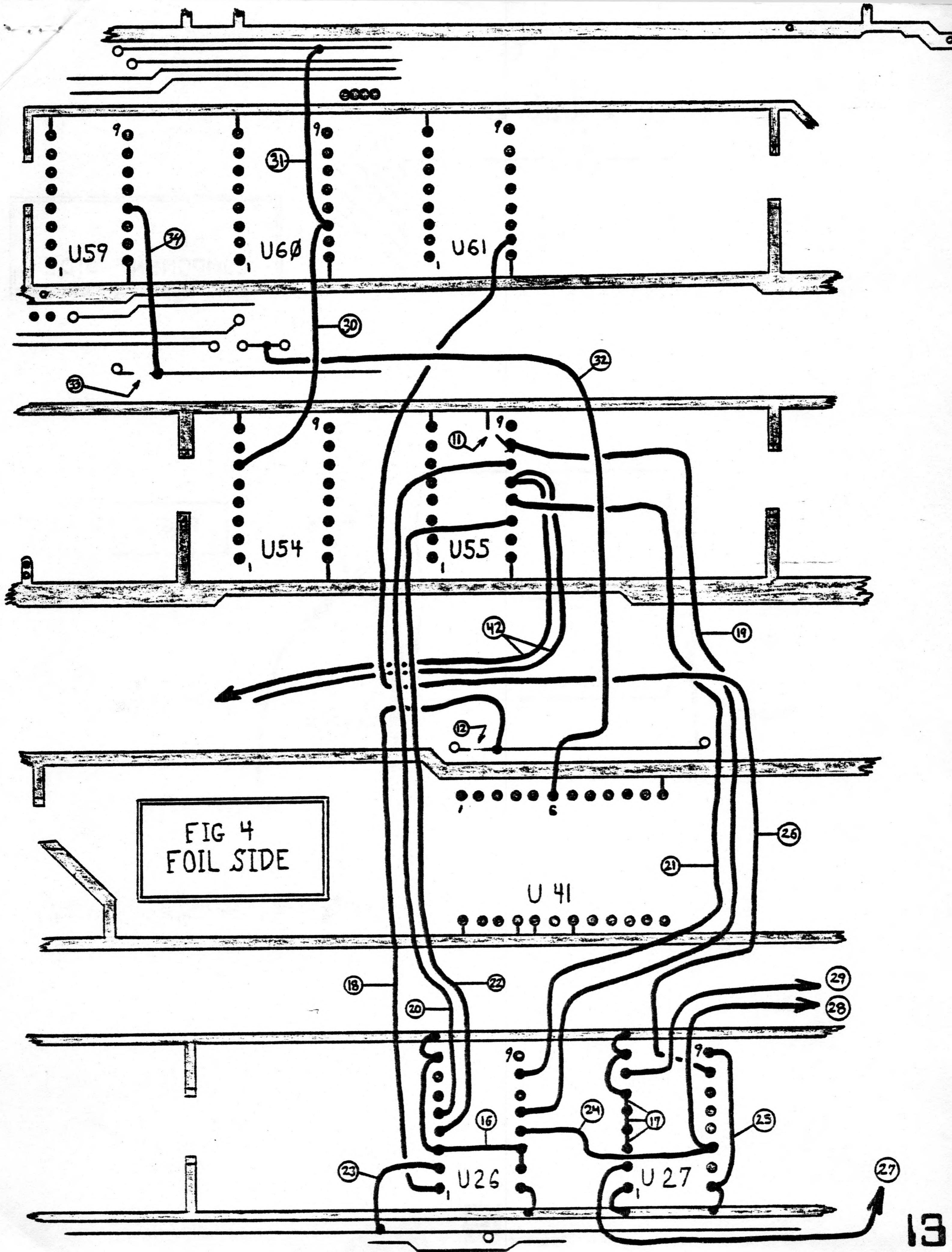

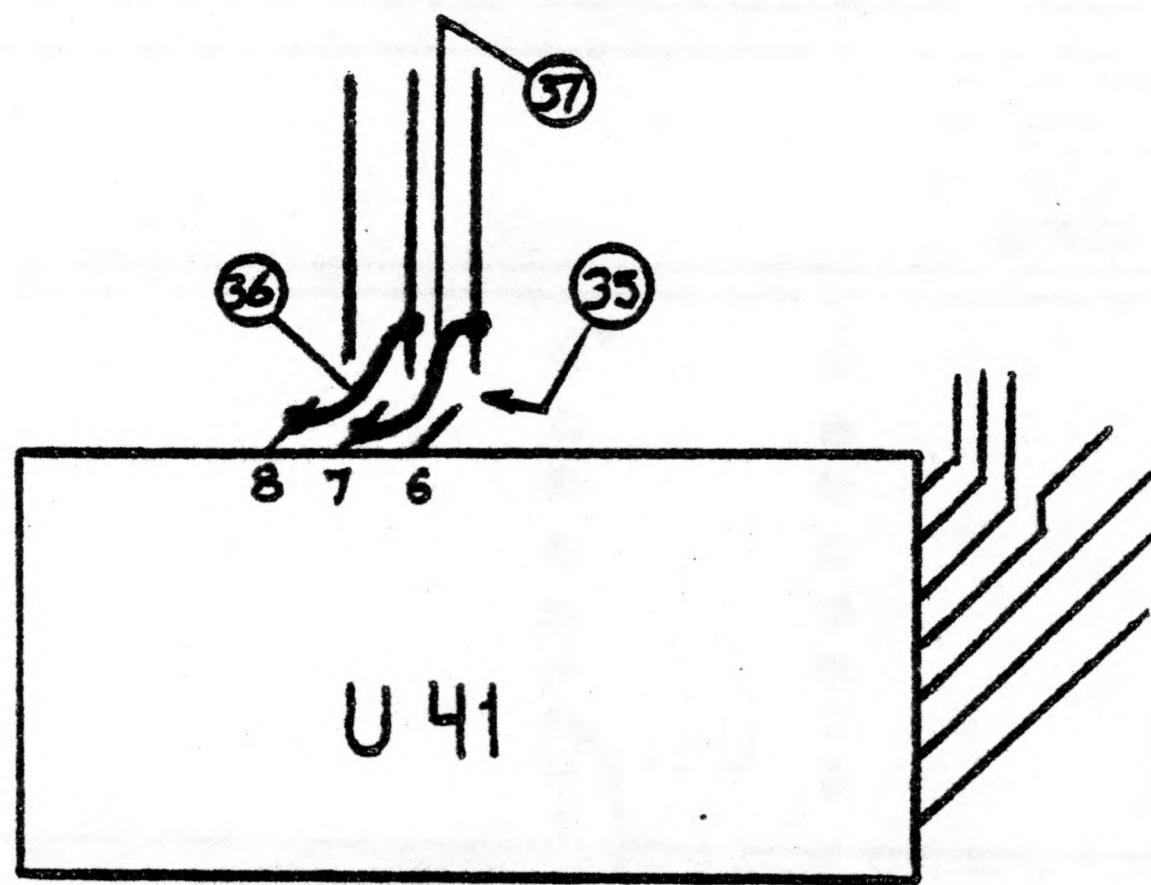


FIG 5
COMPONENT SIDE

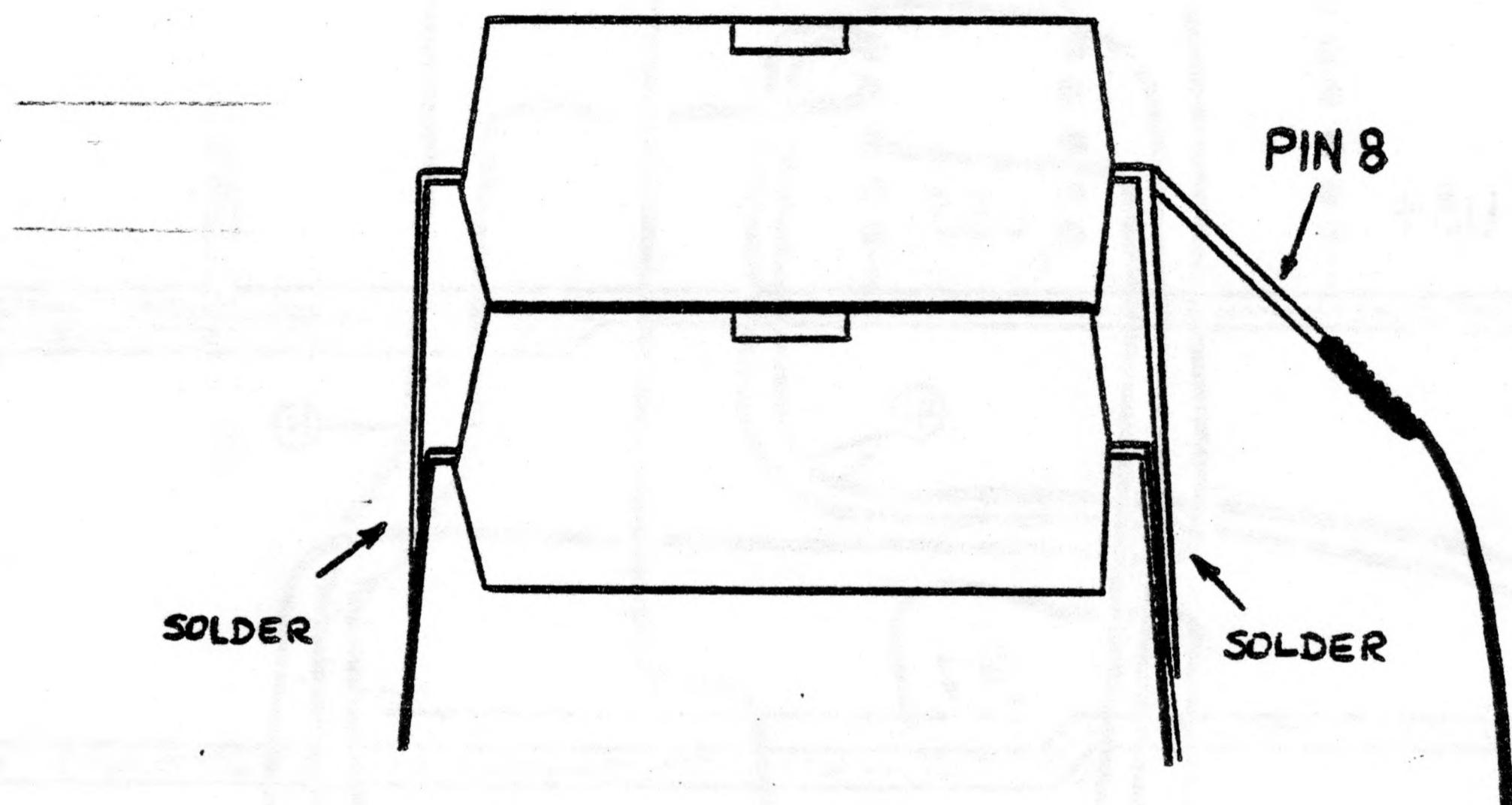


FIG 6